

Instructor: Roman Chomko

LABORATORY # 4 LAB MANUAL

Sequential Logic Design

PART 1 **Flight Attendant Call System**

PART 2 **Rising-edge Detector**

PART 3 **LED Display Time-Multiplexing Circuit***

* Note that in this part of the lab it is required to design a logic circuit and verify its performance ONLY. **DO NOT SYNTHESIZE and realize it on the Basys board.** This will be part of Lab 5 assignment.

Objectives

Lab 4 contains 3 parts: **Part 1** – implementation of a sequential circuit discussed in class; **Part 2** – design and implementation of a state machine; **Part 3** – design of time multiplexing circuits for four-LED display. Its purposes are to get familiar with:

1. Clock synchronous state machine design, synthesis and implementation;
2. Usage of function generator for external “clock” input for Basys FPGA boards via PMOD input/output connectors;
3. Creating and using symbol libraries within Xilinx ISE;
4. Using buses in schematic capture;
5. Vector entries in configuration files, control of external clocks

Equipment

- PC or compatible
- Function Generator (Agilent 33120A)
- Digilent’s Basys Spartan-3E FPGA Evaluation Board

Software

- Xilinx ISE Design Software Suite 10.1
- ModelSim XE III modeling software
- Digilent’s Adept ExPort Software

Parts

- Connecting wires

PART 1. Flight Attendant Call System

In this FPGA application development experiment, we will implement and test the “flight attendant call system” discussed in class using a function generator’s SYNC output as an external driving clock. Use JA-1 PMOD pin for SYNC (clock) input.


Specification

The Flight Attendant System functions according to the following rules:


Flight attendant call button

- Press **CALL**: light turns on
 - ***Stays on*** after button released
- Press **CANCEL**: light turns off

 
And is shown diagrammatically in **Figure 1**.



 *1. Call button pressed – light turns **ON***



 *2. Call button released – light **STAYS ON***



*3. Cancel button pressed – light turns **OFF***

Figure 1. Flight Attendant System State Machine Description

System Analysis and Implementation

As discussed in Lecture 7 from the problem description we can obtain the following state **output/transition table**.

this is a current state

this will be latched
with the rising clock edge

Call	Cancel	Q	D
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table 1. System State Output/Transition Table

Derive **Excitation equation** which leads to the following implementation schematic:

 


Figure 2. Flight Attendant System Schematic

Conduct the Behavioral Simulation.

Digilent Basys Board Implementation Prototype

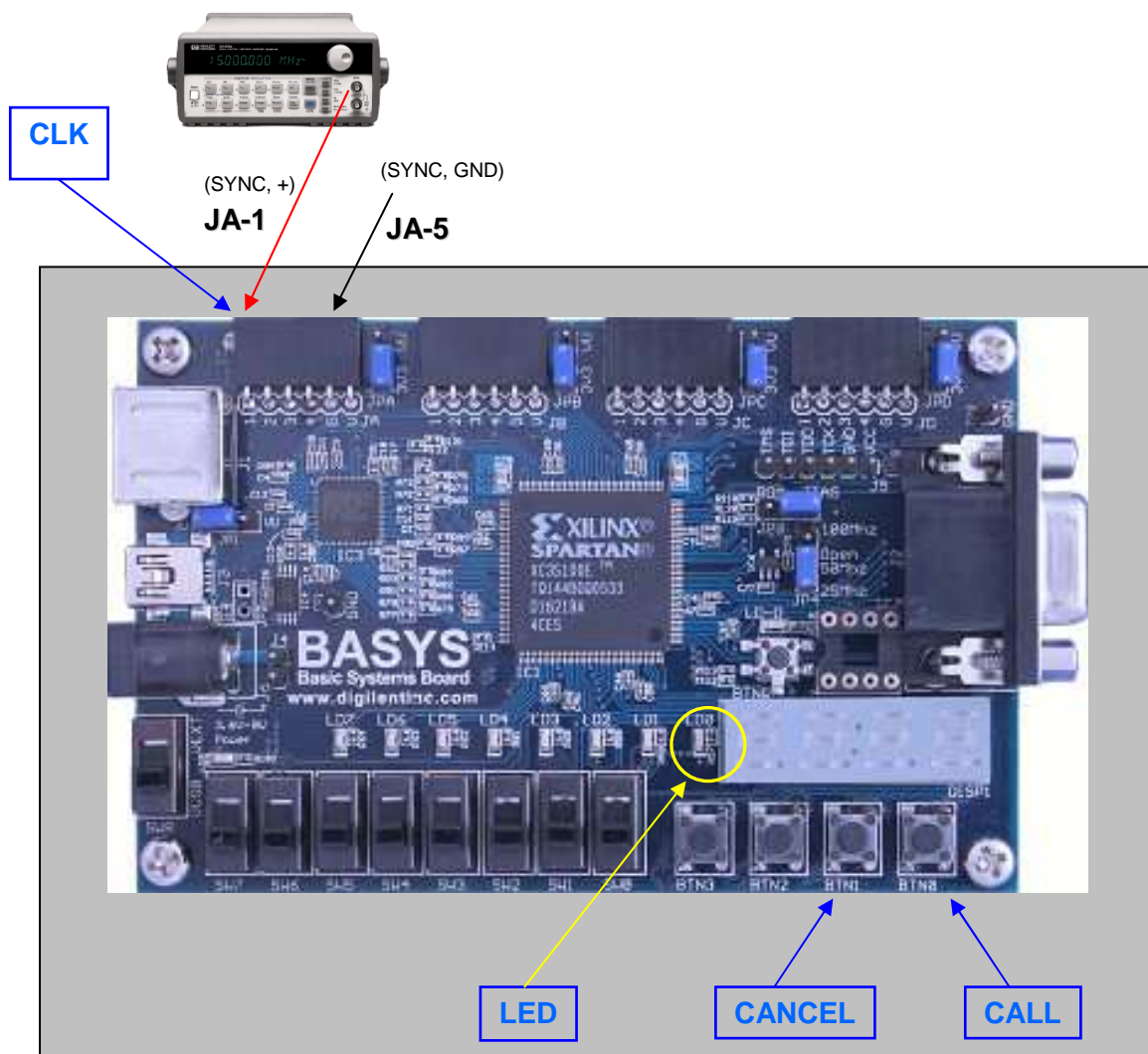


Figure 3. Flight Attendant System Basys Board Set-Up

Synthesis, Mapping and Routing Procedure

Configure the Xilinx ISE project for XC3S100E-TQ144 FPGA on the Digilent's Basys board.

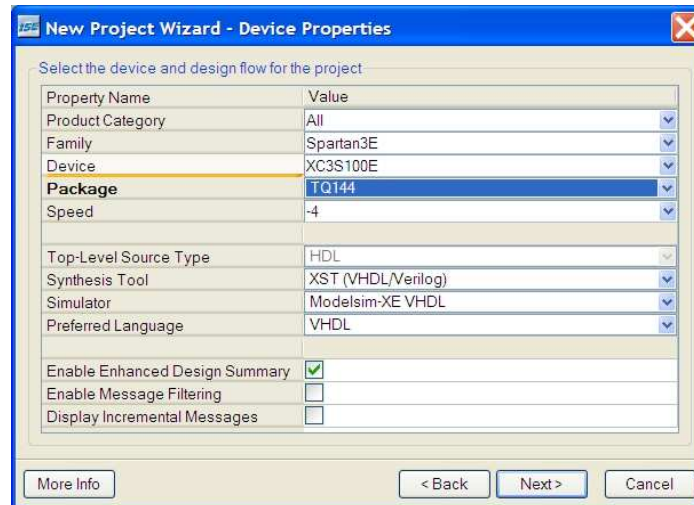


Figure 4. Device Properties Configuration

A function generator Agilent's 33120A SYNC signal is used as an external clock. This however makes Xilinx ISE confused as to how to map and route CLK signal to the D flip-flop in the circuit. The following actions must be taken in order to disable automatic CLK routing procedures:

1. Configuration file must contain the following CLK line which says to ignore any automatic clock routing procedures (no clock)[†]:

```
# PMOD connectors
NET "CLK" LOC = "p81" | CLOCK_DEDICATED_ROUTE = FALSE; # JAl = pin 1, JA5 = GND
```

2. In the Implementation/Map Options ignore user timing constraints:

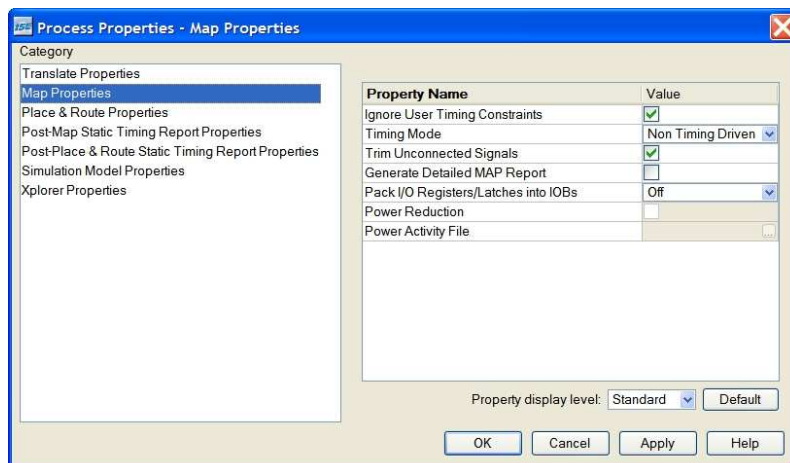


Figure 5. Implementation/Map Configuration

[†] There is a better way to deploy external clocks but it may be confusing for students at this point

3. In the Implementation/Place & Route Options ignore user timing constraints too:

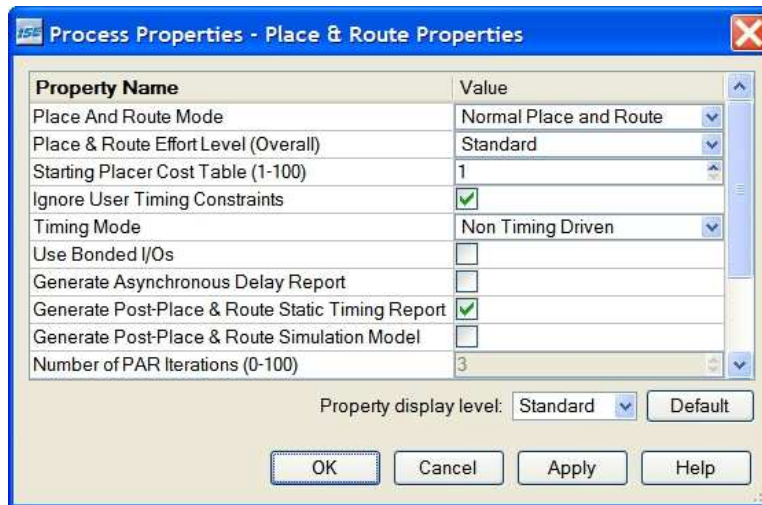


Figure 6. Implementation/Place & Route Configuration

4. ***Ignore*** the resulting ISE WARNINGS. The internal clock will not be used.
5. Make sure that **FPGA startup clock** is **JTAG Clock** (not the default CCLK) in Generate Programming File.

Demonstration

Demonstrate that the application performs according to specs.

Questions

1. What will happen if the “clock” signal is of very low frequency (1 Hz)? Experiment.
2. Design a testbench and verify the logic performance.

PART 2. Rising-edge Detector

Objective

In this assignment it is required to construct a Finite State Machine (FSM) state/output diagram, derive excitation equations and implement it on the Basys Board.

Specification

The rising edge detector is a circuit that generates a short, one-clock-cycle pulse (called a ***tick***) when the input signal changes from '0' to '1'. It is usually used to indicate the onset of a slow time-varying input signal.

NOTE:

1. Use the signal generator's SYNC output for external clocking;
2. Use one of the switches to emulate the input signal;
3. Set clock signal to a sufficiently low frequency to clearly see the LED one-clock-cycle flash

Demonstration

1. Derive a state diagram from the spec's description;
2. Show the output/transition table
3. Derive the excitation equations
4. Design a sequential logic circuit that implements the excitation equation
5. Verify the circuit performance by testbench simulation
6. Implement the application using on-board component of your choice. For clocking procedure use information from PART 1 of the lab above.

PART 3. LED Display Time-Multiplexing Circuit[‡]

Specification

The Digilent Basys Board contains four seven segment LED displays with decimal points. To reduce the number of used of FPGA's I/O pins it is required to use a time-multiplexing sharing scheme. That is, the four displays have their enable signals but share eight common signals to light the segments. All signals are active-low (i.e., enabled when a signal is '0'). The schematic of displaying '3' on the right-most LED is shown in **Figure L4P3-1**.

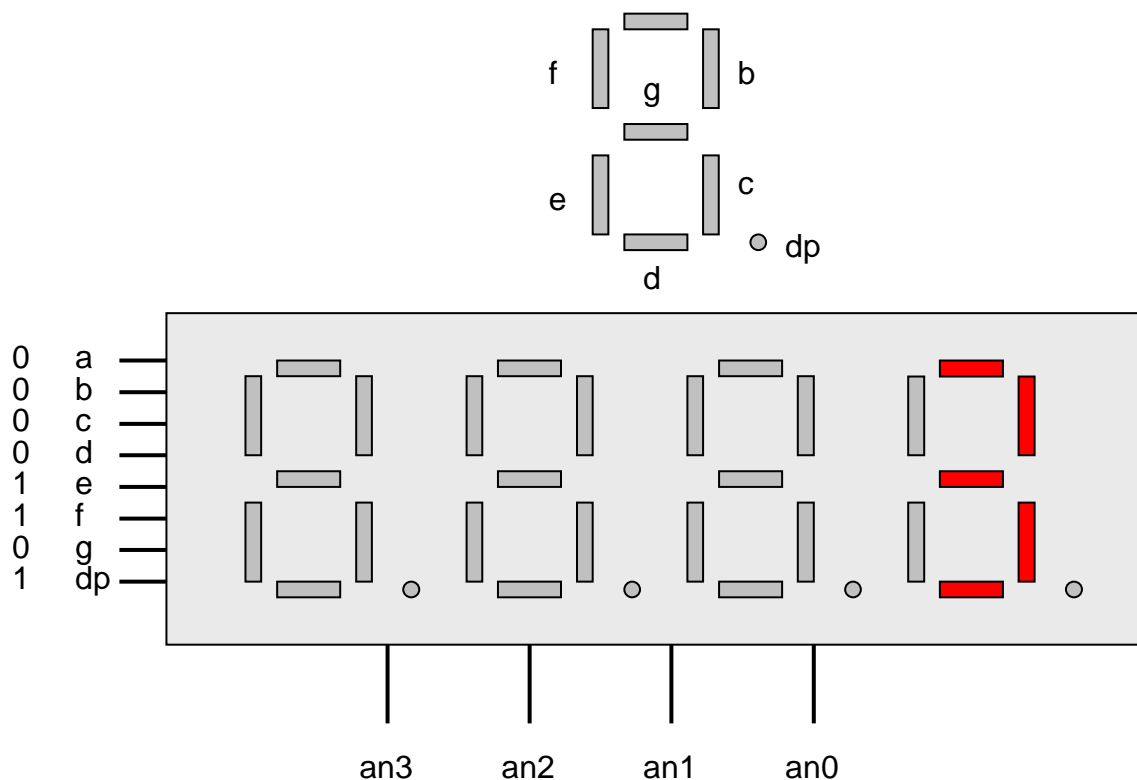


Figure L4P3-1. Displaying '3' on the LED display

Note that the enable signal (i.e., an) is '1110'. This configuration clearly can enable only one display at a time. We can time-multiplex the four LED patterns by enabling the four displays in turn, as shown in the simplified timing diagram in **Figure P4P3-2**. If the refreshing rate of the enable signal is fast enough, the human eye cannot distinguish the on and off intervals of the LEDs and perceives

[‡] Note, in this part of the lab it is required to design a logic circuit and verify its performance ONLY. DO NOT SYNTHESIZE and realize it on the board. This will be part of Lab 5 assignment.

that all four displays are lit simultaneously[§]. This scheme reduces the number of I/O pins from 32 to 12 (i.e., eight LED segments plus four enable signals) but requires a time multiplexing circuit.

 


Figure L4P3-2. Timing diagram of time multiplexing circuit

One of possible realizations is shown in the block diagram of **Figure L4P3-3**. Use it as a guide to implement the circuit and verify (simulate ONLY) its performance.

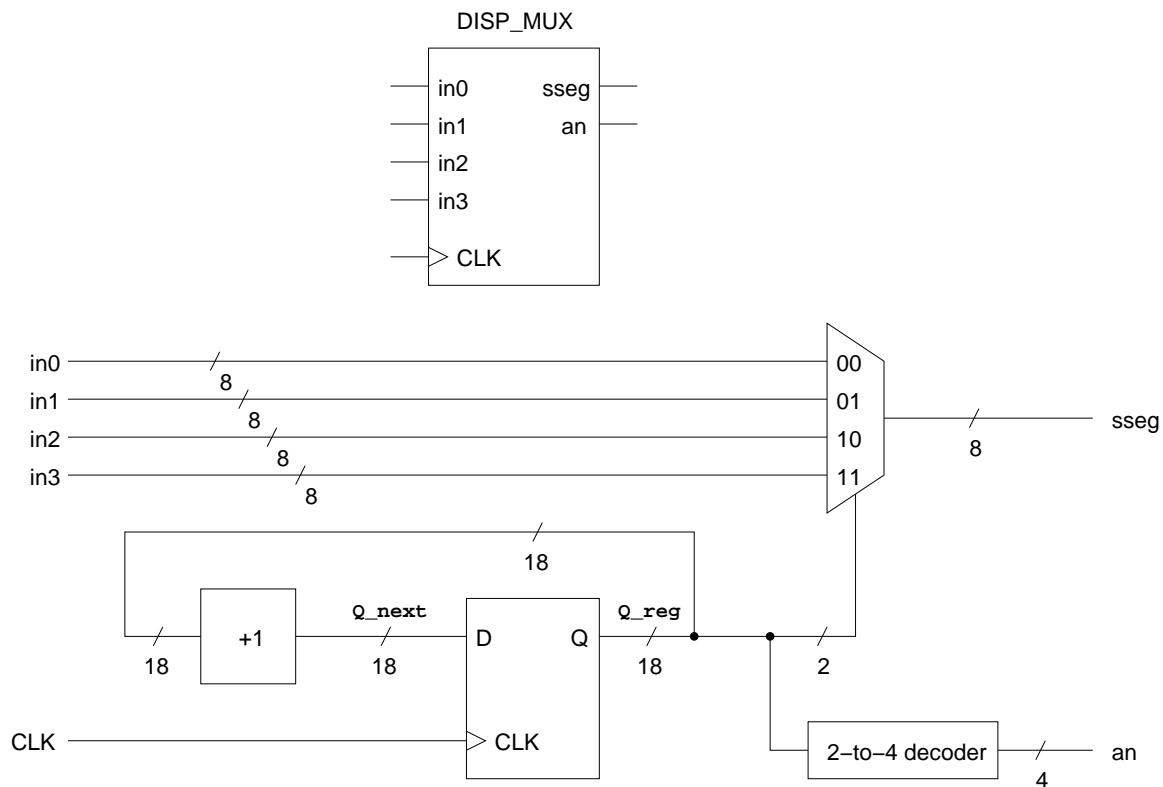


Figure L4P3-3. Symbol and Block diagram of the time-multiplexing circuit

[§] You may have observed damaged traffic lights where LEDs were flickering

Schematic Utility

To expedite correct schematic capture** copy-paste the following VHDL code into a “New VHDL Source Code” and create a schematic symbol for it which can be used to further manipulate the circuit logic.

```

-- -----
-- File:      hex2led.vhd
-- Created:   R.Chomko
-- Date:      2009/01/25
-- Purpose:   decodes Hex (+BCD, +dp) into 7 segment LED Display
--
-- -----

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity HEX_TO_LEDSEG is
    port(
        hex:    in  STD_LOGIC_VECTOR(3 downto 0);
        dp:     in  STD_LOGIC;
        ledseg: out STD_LOGIC_VECTOR(7 downto 0)
    );
end HEX_TO_LEDSEG;

architecture ARCH of HEX_TO_LEDSEG is
begin
    with hex select
        ledseg(6 downto 0) <=
            "0000001" when "0000", -- 0
            "1001111" when "0001", -- 1
            "0010010" when "0010", -- 2
            "0000110" when "0011", -- 3
            "1001100" when "0100", -- 4
            "0100100" when "0101", -- 5
            "0100000" when "0110", -- 6
            "0001111" when "0111", -- 7
            "0000000" when "1000", -- 8
            "0000100" when "1001", -- 9
            "0001000" when "1010", -- a
            "1100000" when "1011", -- b
            "0110001" when "1100", -- c
            "1000010" when "1101", -- d
            "0110000" when "1110", -- e
            "0111000" when others; -- f
        ledseg(7) <= dp;          -- dec.point
end ARCH;

```

Listing 5. HEX-TO-LEDSEG VHDL Code that can also encode DP and Hex Symbols

Demonstration

Demonstrate testbench simulation results and all the supporting material used in designing the system.

** Note that material of Lab 3 can be used if it behaves correctly

Procedures

1. Xilinx ISE Design and Synthesis environment;
2. Creation of Configuration files;
3. Usage of Adept ExPort download software;

Presentation and Report

Must be presented according to the general EE120A lab guidelines posted in iLearn.

Prelab

1. Familiarize yourself with ISE and ModelSim tutorials posted in iLearn;
2. Review Lectures 7-10;
3. Try to answer all the questions, prepare logic truth tables, do all necessary computations